

**A 1GHz 0.134pJ
6-bit Absolute-Value Detector
for use in Neural Spike Sorting**

**Vilius Vysniauskas
Jonathan Hurwitz
Nathan Lee**



Design Summary

- ◆ **Circuit topology:** mixed logic using static CMOS and PTL
- ◆ **Circuit Style:** custom (MUX + carry-out calculator)
- ◆ **Considerations:**
 - Minimized number of transistors and critical path delay
 - Considered wire length and angles for layout
 - Approached problem from design angle, attempting customized logic
- ◆ Best case = **1.0V** for shortest delay, **0.5875V** for lowest energy
- ◆ Worst case = **0.5875V** for longest delay, **1.0V** for highest energy

Delay [ps] (best case)	Delay [ps] (worst case)	Layout Size [μm]	Energy [fJ] (best case)	Energy [fJ] (worst case)	Verification
$t_{p_X0 \rightarrow \text{OUT}} = 371$	$t_{p_X0 \rightarrow \text{OUT}} = 994$	X = 32.48 Y = 21.905	134	397	Func: Yes
$t_{p_X5 \rightarrow \text{OUT}} = 219$	$t_{p_X5 \rightarrow \text{OUT}} = 576$	A = 631 μm^2			DRC: Yes
$t_p = 371$	$t_p = 994$	AR = 1.61			LVS: Yes

Critical Path Analysis

- ◆ **Path elements:** Bit Inversion + Multiplexer + C5 Logic
- ◆ **Total Elements:** 4 INV, 1 T-GATE, 9 NOR, 2 NAND

$$t_{critical} = 4t_{INV} + t_{TG} + 9t_{NOR} + 2t_{NAND}$$


Design Optimization

◆ Critical Path


- From the least significant bit of X to the output C5
- Largest delay occurs because signal travels through the most gates

◆ Sizing Strategy

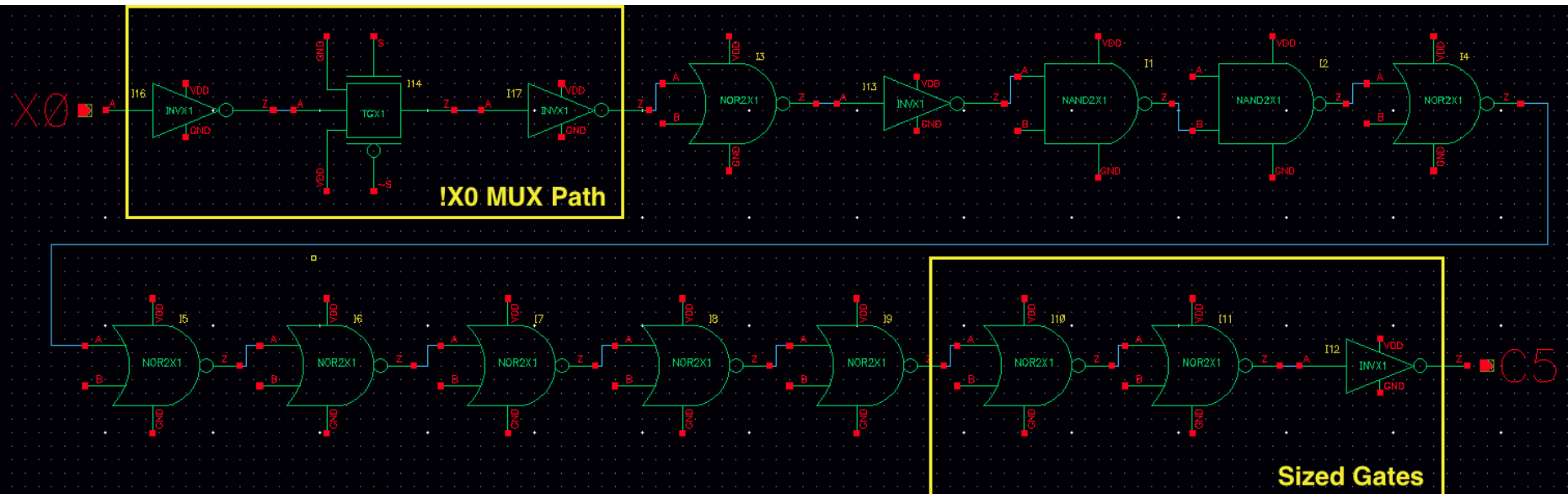- Decrease the size of all FO1 intermediate gates
 - Greatly reduced energy
- Increase size of gates close to output to improve driving capability
 - Reduction in delay
- Experimented with different gate sizing based on simulation result
 - Further improved results



Functionality Check

 


Layout

X [μm]	Y [μm]	A [μm^2]	AR
32.48	21.905	631	1.61

◆ Area Calculation

 - Defined as $X*Y$, but with void space around perimeter removed
 - Approximately $80 \mu\text{m}^2$
- Chose to minimize total area and wire length
 - Width decrease
 - Aspect ratio increase



Discussion

◆ Three most important features

- Eliminated need for separate adder (to create $|x|$)
- Used carry look-ahead logic to combine absolute value calculation and comparator logic into one stage
- Efficient, high-level design minimized transistor count

◆ Things to consider for next time

- Customized design and cell density greatly increased layout complexity
- Non-uniform cell size complicated area calculations